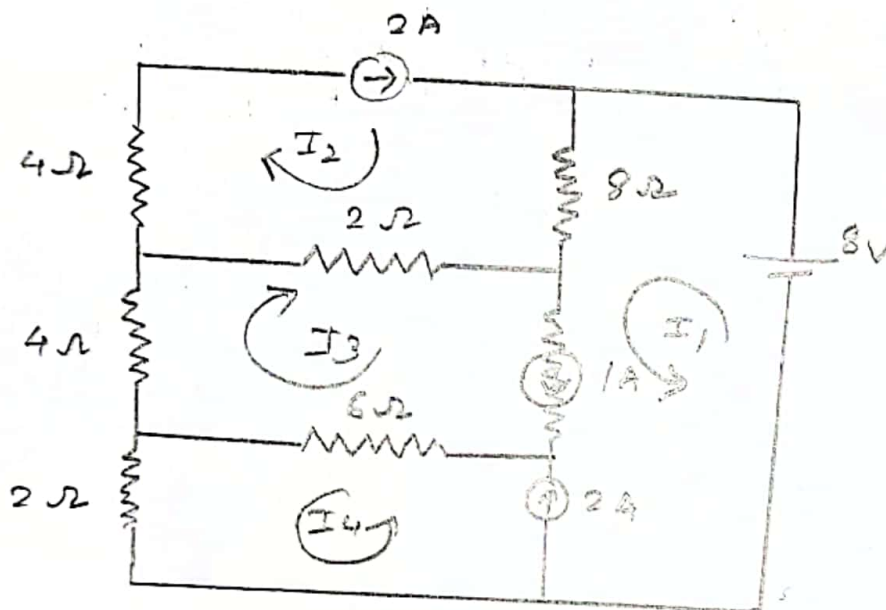


Q1) For the circuit in fig 1. Find the following.

- A) The power supplied/absorbed by the 8V source is 80.32W
B) The power absorbed by the 8Ω resistor is 32W
C) The voltage across the 6Ω resistor is 15.18V



MESH 4

$$-16 - 8I_4 - 6I_3 = 0$$

$$3I_3 + 4I_4 = -8 \quad (4)$$

$$I_1 = 10.04A$$

$$I_2 = -8.04A$$

$$I_3 = -2.14A$$

$$I_4 = 0.39A$$

A1) MESH 1

$$8 - 8 + 16 - 8(I_2 + I_2) = 0$$

$$I_1 + I_2 = 2 \quad (1)$$

MESH 2

$$-28 - 8(I_2 + I_1) - 4I_2 - 2(I_2 - I_3) = 0$$

$$\Rightarrow -14 - 7I_2 - 4I_1 + I_3 = 0$$


$$4I_1 + 7I_2 - I_3 = -14 \quad (2)$$

MESH 3

$$-12 - 12I_3 + 2I_2 - 6I_4 = 0$$

$$I_2 - 6I_3 - 3I_4 = 6 \quad (3)$$

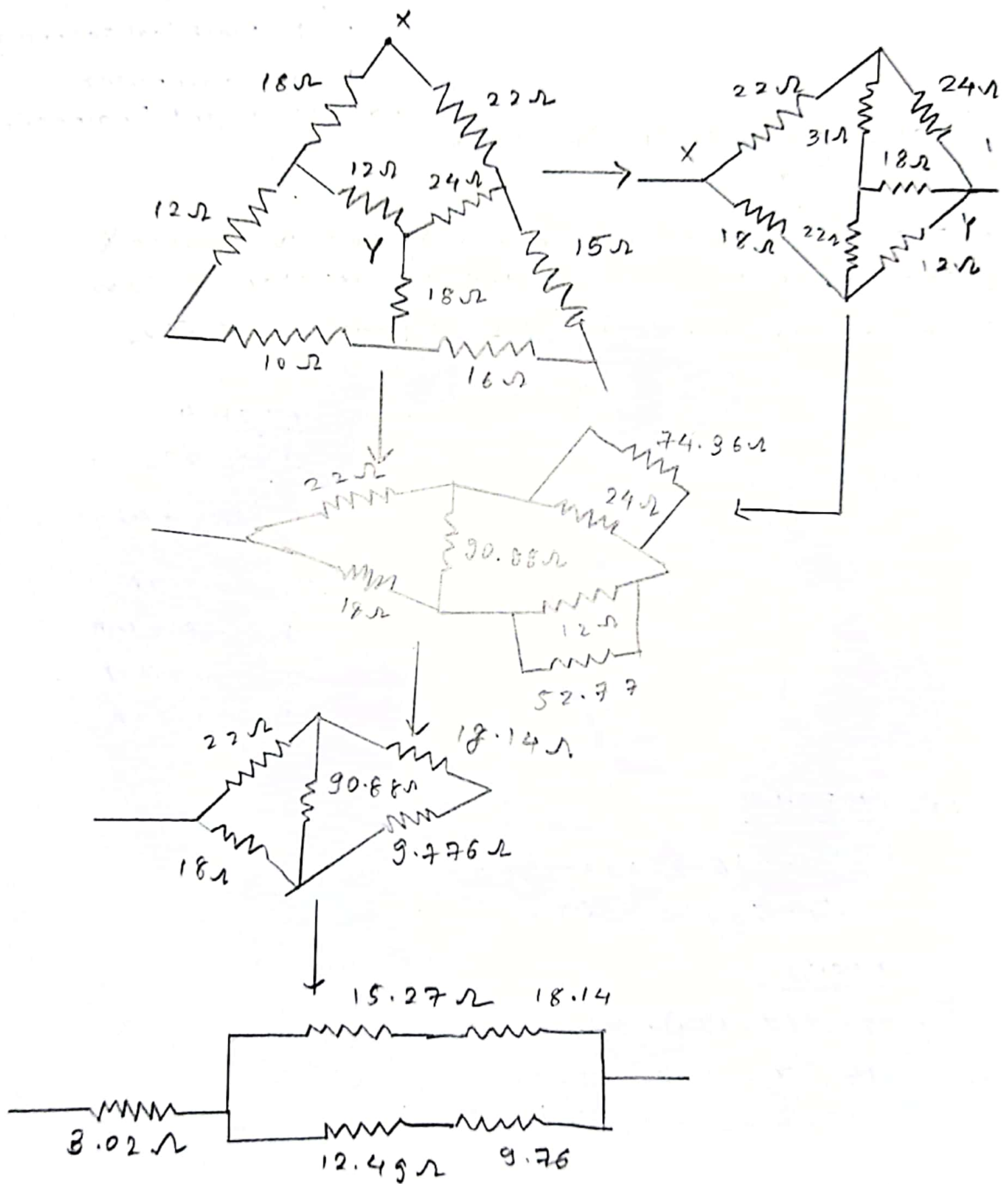Q2) The equivalent Resistance between terminals X and Y of the circuit in Figure is









$$R_{eq} = 16.381\Omega$$


Q2) b. For the circuit shown in Figure 8 Find the Thevenin parameter to determine the following; w.r.t

A) Thevenin's voltage (V_{TH}) is?

B) Thevenin's resistance (R_{TH}) is?

C) power dissipation in R_L resistor is?

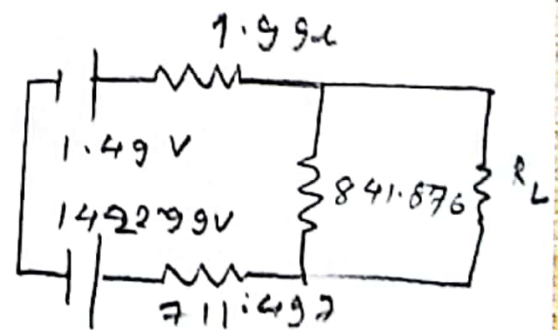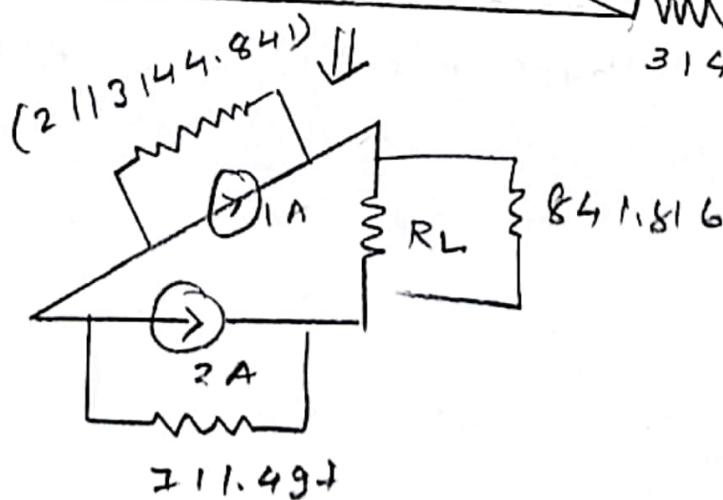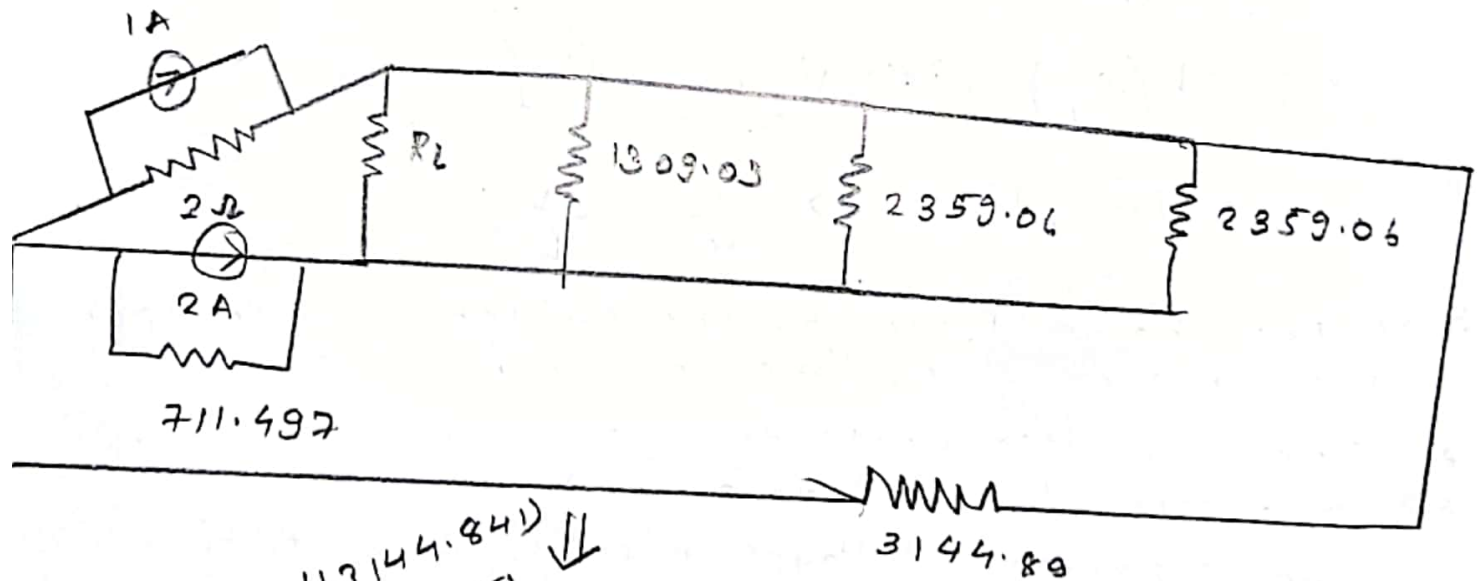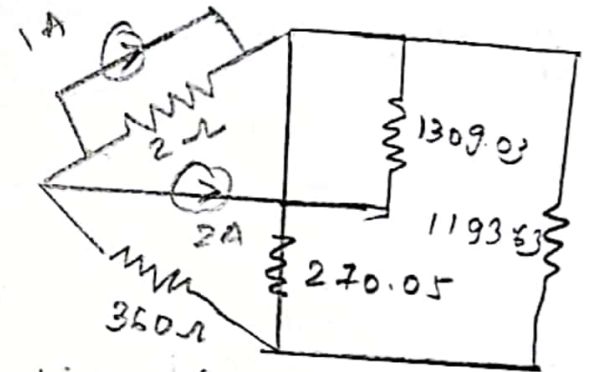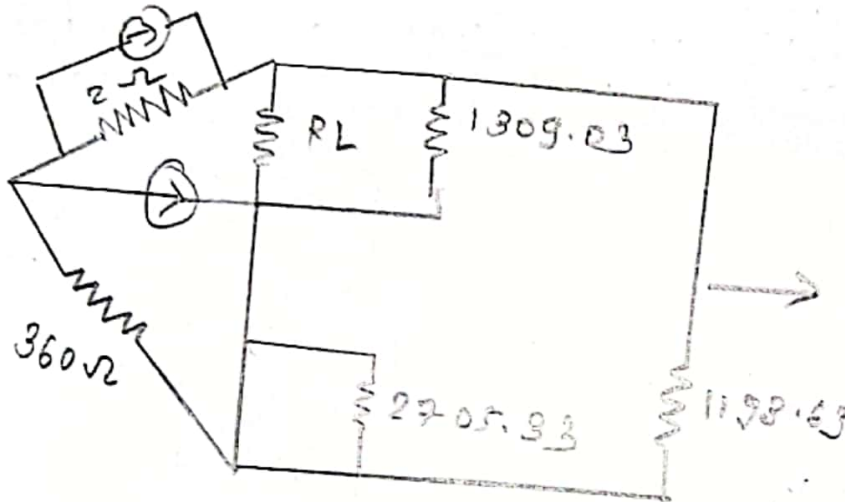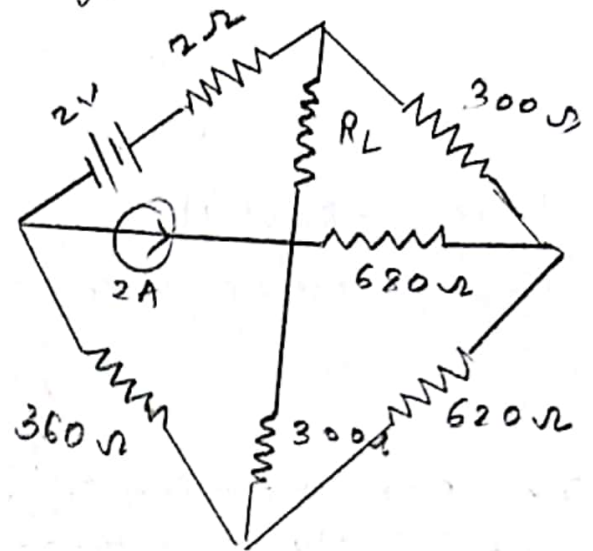

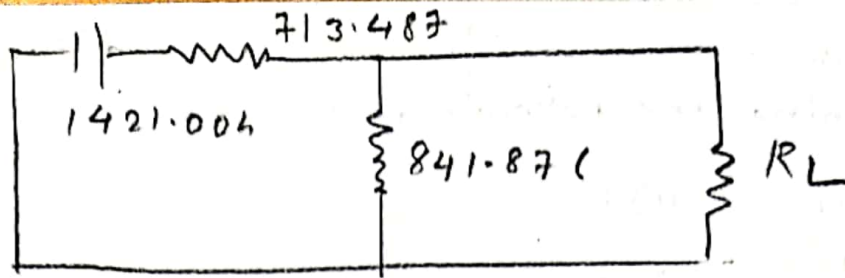


$$R_{TH} = 386.191 \Omega$$

$$V_{TH} = 1421.004$$

$$P_{TH} = \left(\frac{1421.004}{386.191 + R_L} \right)^2 R_L$$

$$= \frac{2.01 \times 10^4 R_L}{386.191 + R_L}$$

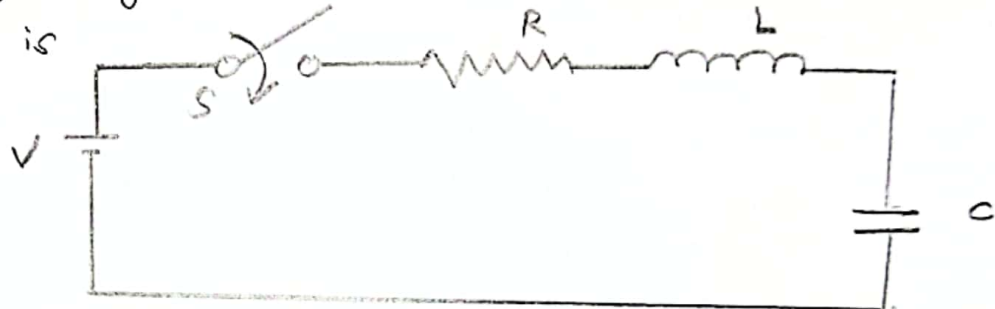Q5) a) For the circuit, assuming switch was open for sufficiently long time and then closed at $t=0$ - the $\frac{di}{dt}$ at $t=0^+$ is




$$V = L \left(\frac{di}{dt} \right) + iR + v_C$$


$$V = L \left(\frac{di}{dt} \right) + iR + V [1 - e^{-t/RC}]$$

$$0 = L \left(\frac{di}{dt} \right) + iR \Rightarrow \frac{di}{dt} = -\frac{V}{L}$$

Q3 b) For the in Figure 5, the switch was in open position for a long time, and then operated

- The capacitor voltage at $t=0$ is?
- The capacitor at $t=\infty$ is?
- The capacitor voltages because x V at time?

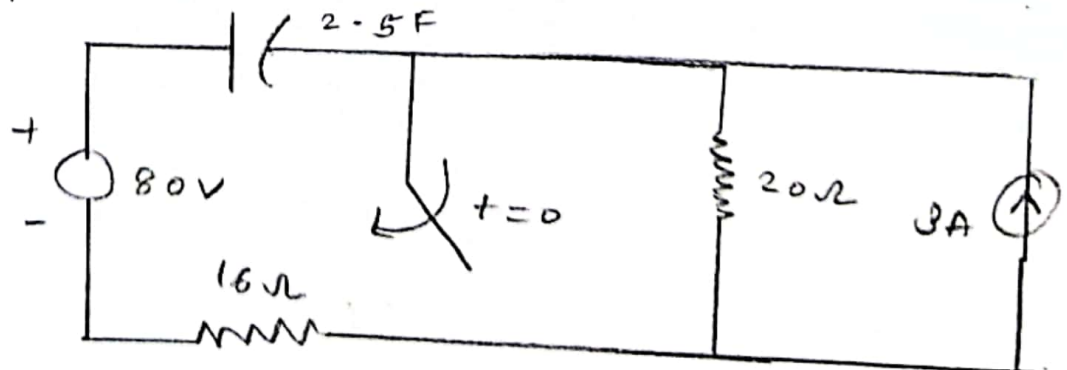

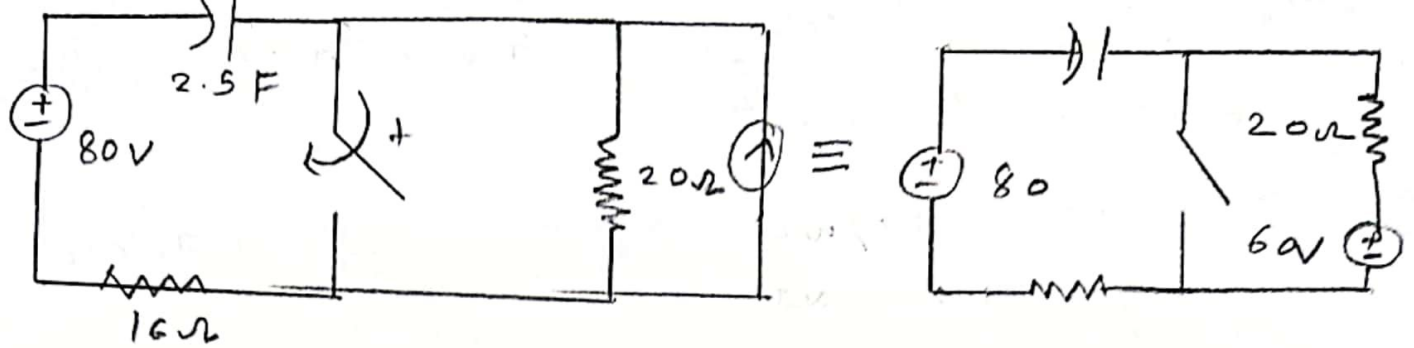

Ans 1) at $t=0$, capacitor is a wire $\Rightarrow V_C = 20V$

2) at $t=\infty$ capacitor is open ckt $\Rightarrow V_C = 80V$


$$3) \quad xV = V [1 - e^{-t/RC}]$$

$$\frac{-t}{RC} = \ln(1-x)$$

$$t = -40 \ln(1-x)$$

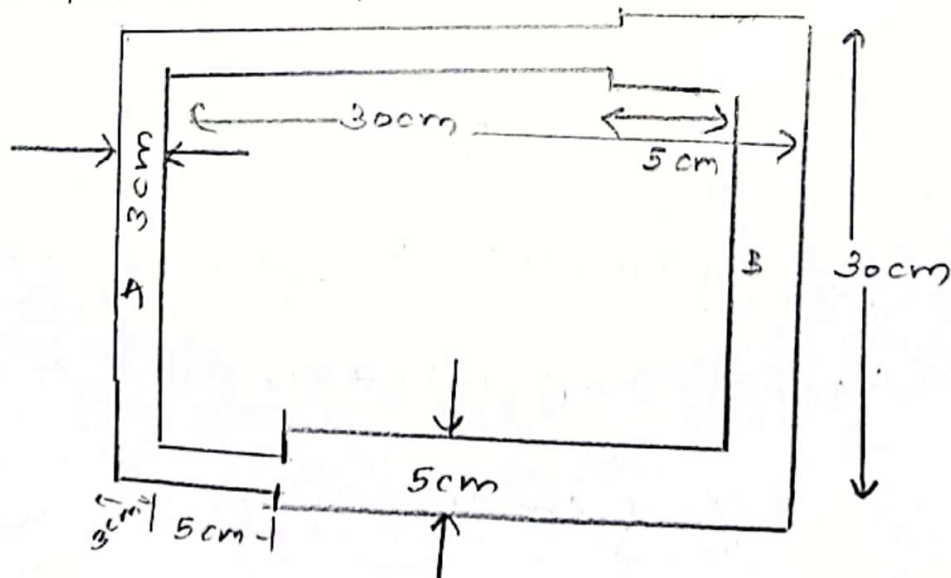Q4) A core, having square-section, is shown. It is made of two ferromagnetic materials, A and B with a relative permeability of 600 and 1200 resp.

Ans A) A coil of N turns is wound on the core. The current required in the coil to produce a flux of x Wb is



$$\text{Ans A) } l_A = 22 + 1.5 + 1.5 + 1.5 + 5 + 1.5 + 17 = 50 \text{ cm} = 0.5 \text{ m}$$

$$l_B = 20 + 2.5 + 2.5 + 17 + 2.5 + 17 + 2.5 = 52 \text{ cm} = 0.52 \text{ m}$$

$$A_A = 9 \times 10^{-4} \text{ m}^2$$

$$A_B = 25 \times 10^{-4} \text{ m}^2$$

$$S_A = \frac{l_A}{\mu_0 \mu_r A_A} = \frac{0.5}{600 \times 4\pi \times 10^{-7} \times 9 \times 10^{-4}} = 0.736 \times 10^6 \text{ AT/Wb}$$

$$S_B = \frac{0.52}{1200 \times 4\pi \times 10^{-7} \times 25 \times 10^{-4}} = 0.137 \times 10^6 \text{ AT/Wb}$$

$$S_{eq} = 0.873 \times 10^6 \text{ AT/Wb}$$

$$\phi \times S_{eq} = \text{MMF} = NI$$


$$S_{eq} = \frac{0.002}{4\pi \times 10^{-7} \times 9 \times 10^{-4}} = 1.76 \times 10^6 \text{ AT/Wb}$$

$$\left(\frac{0.87 \times 10^6}{\gamma} \right) A = I \quad S_{eq}' = 2.63 \times 10^6 \text{ AT/Wb}$$

$$c) \text{ convert } S_{eq} = \frac{X}{\gamma} (2.63 \times 10^6)$$

Q5) Determine the following

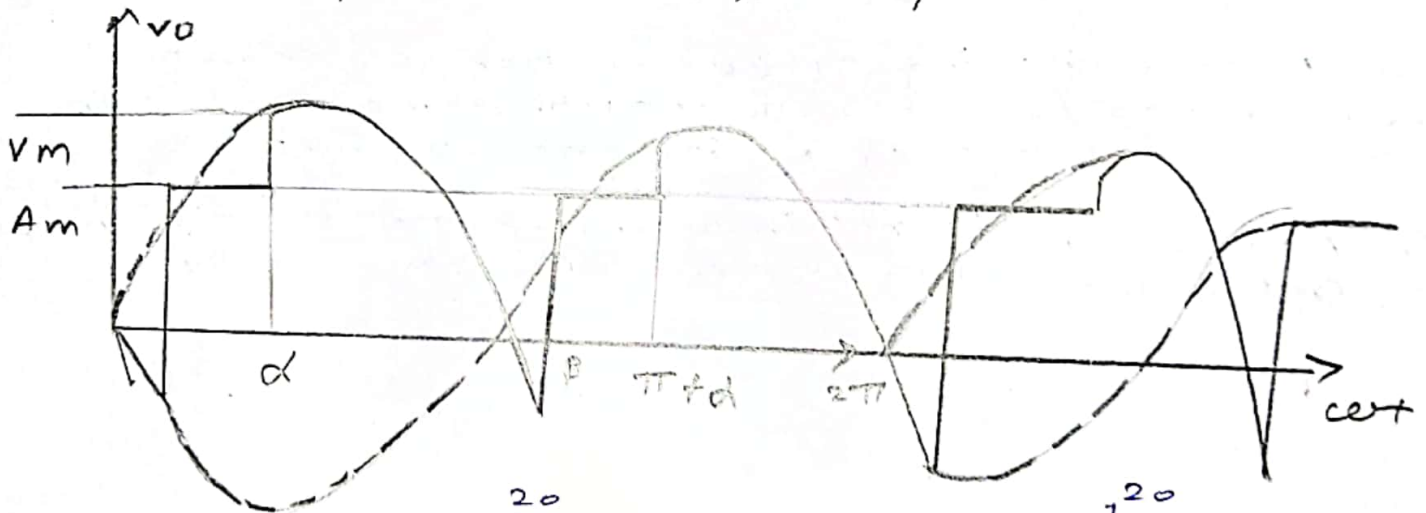A) Determine the average value of the waveform if $\alpha = 75^\circ$, $\beta = 200^\circ$, $V_m = 1$, $A_m = 4$



$$\text{part I} := \frac{-1}{40} \int_0^{20} V_m \sin \theta \cdot d\theta = \frac{-V_m \cos \theta}{40} \Big|_0^{20} = \frac{V_m}{40} (\cos 20 - 1)$$

$$V_{avg} = -V_m f (1.507 \times 10^{-3}) V$$

part II

$$V_{avg} = \frac{1}{40} \int_0^{55} A_m dt = \frac{A_m 55}{40} = 0.54 \text{ sec}$$

part III

$$V_{avg} = \frac{V_m}{210} \int_0^{105} \sin \theta \cdot d\theta = 5.99 \times 10^{-3} V_m$$

$$V_{avg} = 0.54 + 4.487 \times 10^{-3} V_m$$

B) Determine the rms value of the waveform if $\omega = 50$
 $P = 2000$, $V_m = x$, $A_m = y$

RMS
part I : $\sqrt{\frac{1}{40} \int_0^{20} V_m^2 \sin^2 \theta \cdot d\theta} = V_m (0.498)$

part II : $\sqrt{\frac{1}{110} \int_0^{55} A_m^2 dt} = \frac{A_m}{\sqrt{2}}$

part III : $\sqrt{\frac{1}{210} \int_0^{105} V_m^4 \sin^4 \theta \cdot d\theta} = V_m (0.5)$

$$V_{RMS} = 0.996x + 0.707y$$

Q6) Three circuit A, B and C are connected in parallel across a single phase AC supply

- a) A consists of bank of lamps in a 10 A at unity power
- b) B consists of a coil taking of 20 A to power of 0.8
- c) C consists of a resistor & capacitor in series, taking a current of 10 A at a power factor of 0.9

Ans 6) A) $P_A = V_A I_A \Rightarrow V_A = 200V$

as all 3 are in || $V_A = V_B = V_C = V_{Supply} = 200V$

c) $P_{supplied to A} = V_A I_A = 2000W$ $PFA = 1$
 $P_A = 2000$

$P_{supplied to B} = V_B I_B = 4000W$ $PFB = 0.8$
 $P_B = 3200W$

$P_{supplied to C} = V_C I_C = 2000W$ $PFC = 0.9$
 $P_C = 1800W$

$P_{total} = 7000W$

d) $PF = \frac{7}{8} = 0.875$

Q7) 3 similar coils, each having a resistance of 8Ω & an inductive reactance of 8Ω are connected in star across a $415V$, 3 phase, 50 Hz supply calculate " action -

$$\text{Ans 7) } Z = \sqrt{(8)^2 + (8)^2} \Omega = 8\sqrt{2} \Omega = 8 + 8i$$

$\angle 45^\circ$

$$V = \frac{415}{\sqrt{3}} = 239.6V$$

$$I_2 = \frac{V}{Z} = \frac{239.6}{8\sqrt{2}} = 21.177A$$


$$\text{PF} = \cos\phi = 1/\sqrt{2}$$

$$\text{Active power} = \sqrt{3} V I \cos\phi = 6214.36W$$

$$\text{Reactive power} = \sqrt{3} V I \sin\phi = 6214.36W$$

$$\text{Apparent power} = 8788.44W$$

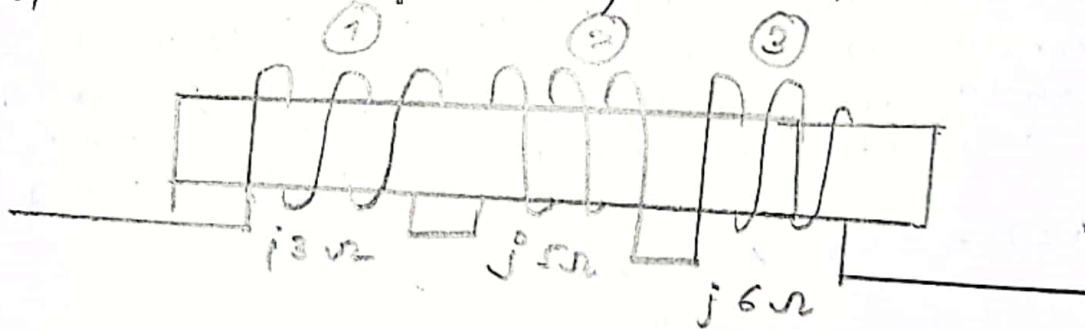Q8) The following ckt is supplied from a 50 Hz source with current enter from R.H.S. Draw the dotted eqt ckt and determine the eq inductance if coeff of coupling b/w coils 1 & 2 & coils 2 & 3 is 0.7



A8)

$$L_1 = 3 / (2\pi \times 50) = 9.55mH$$

$$L_2 = 5 / (2\pi \times 50) = 15.92mH$$

$$L_3 = 6 / (2\pi \times 50) = 19.1mH$$

$$M_{12} = 8.63 \times 10^{-3} \quad M_{23} = 12.2 \times 10^{-3} \quad M_{13} = 5.4 \times 10^{-3}$$

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} + 2M_{13}$$

$$L_{eq} = 13.71mH$$

Q9) 3 phase star connected balanced load has an impedance of $Z = (8 + j6) \Omega$ per phase. If load is connected to 3-phase 208V

Ans 9) $Z = 8 + j6 = 10 \angle 37^\circ$

$V_L = 208V$

$V_{ph} = \frac{208}{\sqrt{3}} \quad V_m = 120.08V$


$I_L = 12.008A$

Active power = $\sqrt{3} V I \cos \phi = 1994.576W$

Reactive power = $\sqrt{3} V I \sin \theta = 1503.02W$

Apparent power = $2497.479W$

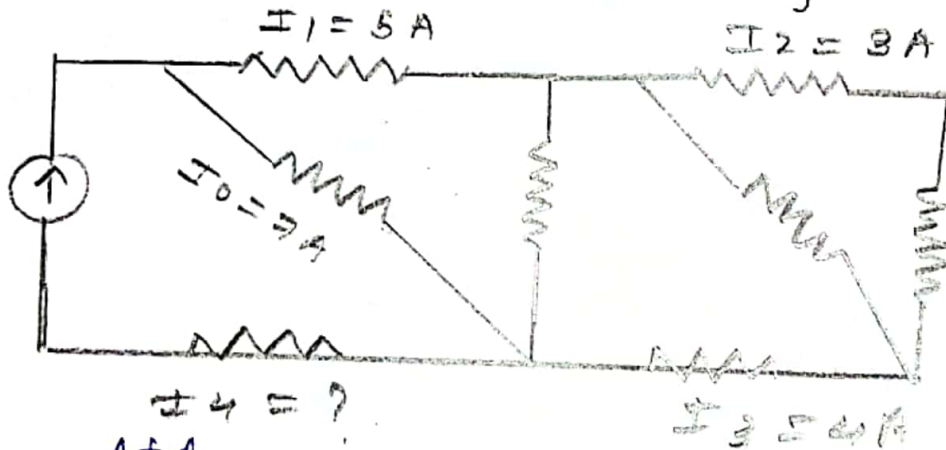Q10) The current I_4 in the following ckt is equal to:-



A10) $\frac{A+B}{I_1 = 3+7 = 10A}$

$\frac{A+C}{I_2 + 5 + 3 = I_1 \Rightarrow I_2 = 2A}$

$\frac{A+B}{7 + 7 + I_4 = I_2 \Rightarrow I_4 = -12A}$

~~I_4~~